

# Digital Electronics 101

An introductory course on Electronics, C++ and Arduino-like platforms

J. Rodrigues   R. Antunes

HackerSchool

## What are Electronics?

---

# Fundamental Notions and Laws in Electronics

There are three main notions to be understood in electronics:

- **Current aka  $I$**  (SI: Ampere): The ordered flow of electrons, therefore electrical charge per time unit
- **Electrical Tension or Potential Difference aka  $U$**  (SI: Volt): The tension applied on said electrons, therefore energy per charge
- **Resistance aka  $R$**  (SI: Ohm): The resistance of a medium to the electron flow

# Ohm's Law

We can describe the resistance as the tension we have to “apply” to push the electron flow establishing an equality-**Ohm's Law**:

$$R = \frac{U}{I}$$

Or in a funnier way:


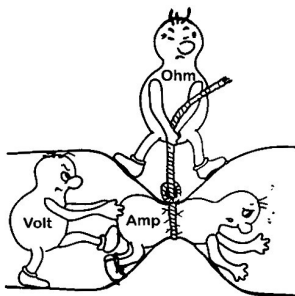


Figure 1: Ohm's Law
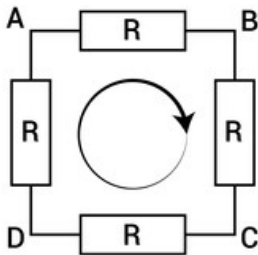
# Kirchhoff's Voltage Law

*The sum of all potential differences in a loop is zero!*



$$V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0$$

Figure 2: Kirchhoff's Voltage Law

# Kirchhoff's Current Law

*There can be no residual current in a node!*

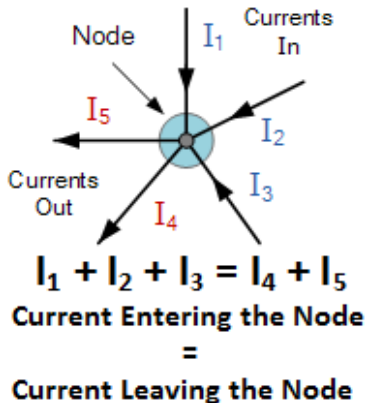


Figure 3: Kirchhoff's Current Law


# Additional Notions and Fundamentals

Then we can also add some additional notions

- **Power**(SI: Watt): Rate of transference of electrical energy through a circuit, using the definition of Electrical Tension and current:

$$P = U \times I$$

# Breadboards and PCBs I

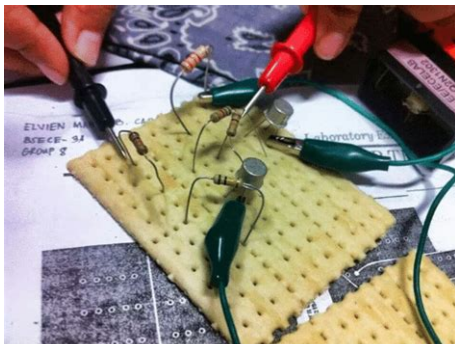

Use a breadboard they said..

Figure 4: A BREADboard!



## Breadboards and PCBs II

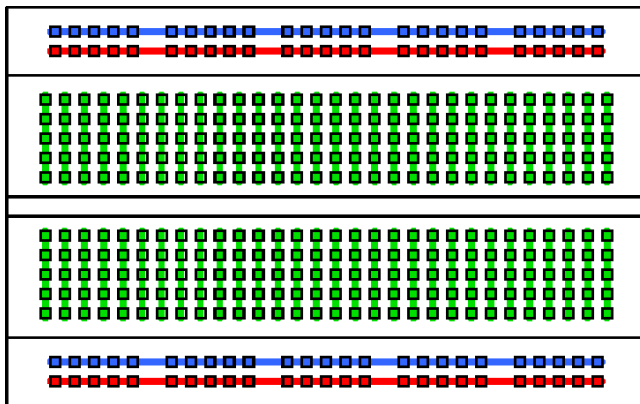


Figure 5: An actual breadboard

## Breadboards and PCBs III

After testing our circuit in a breadboard, we might have a very complex and not portable weave of wires and components. . .

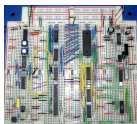


Figure 6: A very confusing weave of wires

We can then use some software tools (like KiCAD) to help us create a PCB schematic. After that we can send it to a manufacturer or do it ourselves!

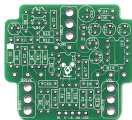


Figure 7: A printable circuit board

# Power sources

The most fundamental devices are power sources. They supply (active component) a given tension to our circuit through the conversion of an x type of energy (chemical, mechanical, etc.) into electrical energy.

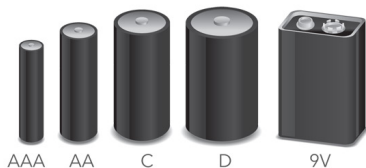


Figure 8: Batteries - A conversion device of chemical into electrical energy

# Resistors

Another fundamental component. Depending on the resistor type they introduce a fixed or variable resistance ( $R$ ) into our circuits. They are unpolarized.

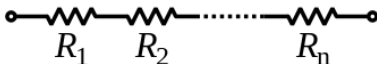


Figure 9: Series association:  $R_{eq} = R_1 + R_2 + \dots + R_n$

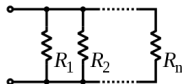


Figure 10: Paralel association:  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$

# Resistors II

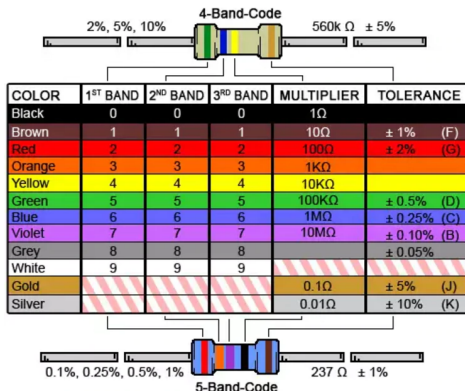


Figure 11: How to read a resistor

# Toggle Components

They toggle the loop where they are placed, opening or closing said loop.



Figure 12: A press button and a toggle switch

# Capacitors in a DC circuit

Capacitors are components with relevant capacitance.

- **Capacitance**(SI: Farad): The ability of a material to store electrical charge. In a DC circuit:

$$C = \frac{q}{U}$$

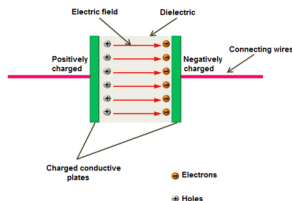


Figure 13: A capacitor schematic

Why is this relevant?...

## A practical example - the RC circuit

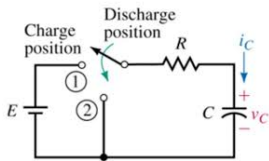


Figure 14: A resistor-capacitor circuit

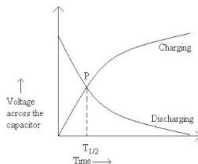


Figure 15: The capacitor's charge and discharge graphs with  $\tau = RC$

And capacitors have many more appliances such as filtering, shielding, etc.



# Diodes

Diodes are components that limit the flow of electrical current in a single orientation. Nowadays most diodes are composed of semiconductors in a p-n junction, which is also the material basis for another important component, the **transistor**.

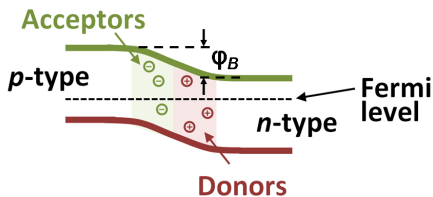


Figure 16: P-N junction

Diodes have a limited use in DC circuits, however we can use them to protect other components from inverted polarity, to construct diode logic gates, etc., or...

# LEDs

Arguably the most used diodes in DC circuits.

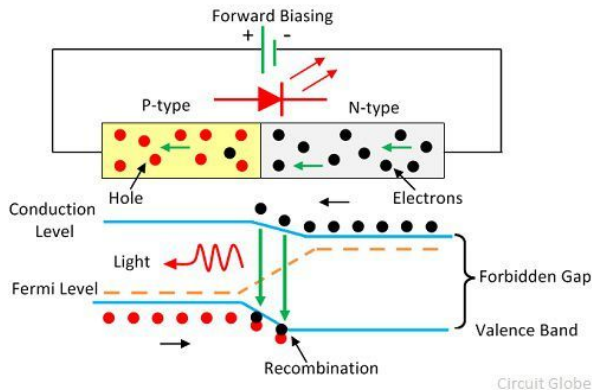


Figure 17: The inner workings of a LED

# Integrated Circuits

Integrated circuits have a myriad of functions from amp-ops, to integrated diodes, to timers and even logic gates. They are composed of tiny MOSFE transistors.



Figure 18: The Signetic's 555 timer IC

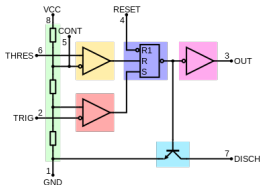


Figure 19: Logic diagram of the 555 timer

# Integrated Circuits II

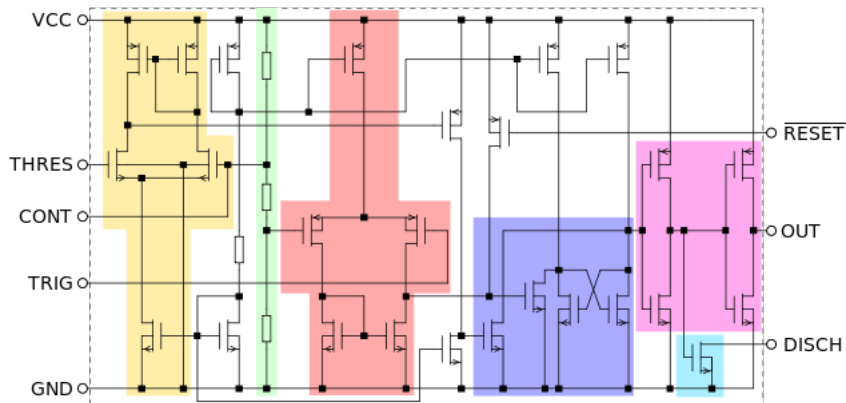


Figure 20: CMOS diagram of the 555 timer

# Arduino

Arduino boards are microcontrollers under a CC-BY-SA license.

They allow the integration of digital and analog control, UART bus communication, etc. into electronic circuits, expanding their potential.

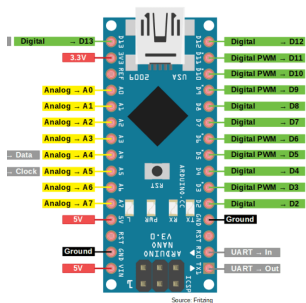


Figure 21: Arduino Nano pinout

# Arduino IDE

The Arduino IDE, is an integrated development enviroment under LGPL. It allows serial communication with a Arduino board, compilation of .ino files (based on C++) and flashing of said binaries into a Arduino Board. Recently a 2.0 version of the IDE has been released.

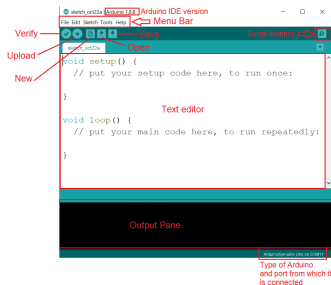


Figure 22: Arduino IDE

# Controlling your Arduino with C++